

Lab 03

Handout#03: Behavioural Modelling for Combinational Circuits

1. Encoders are opposite to decoders, and are supposed to generate coded outputs from a single active numeric input. A Decimal to BCD Encoder takes 10 inputs and generates corresponding 4-bit outputs.

- a. Design truth table for the decimal to BCD encoder.

Lab 03

Q No 1:

y_9	y_8	y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0	A_3	A_2	A_1	A_0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	0	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

$A_0 = y_0 + y_1 + y_2 + y_3$

- b. Derive the Boolean expression, and simplify if possible.

$$\begin{aligned}
 A_0 &= y_1 + y_3 + y_5 + y_7 \\
 A_1 &= y_2 + y_3 + y_6 + y_7 \\
 A_2 &= y_4 + y_5 + y_6 + y_7 \\
 A_3 &= y_8 + y_9
 \end{aligned}$$

- c. Implement the design using Verilog behavioural modelling, and provide code screenshot.

```

21
22 // Malak Majeed Ullah khan
23
24 module DEC_BCD(out, SW);
25 //Dimension and sizes
26 input wire [9:0] SW;
27 output reg [3:0] out;
28
29 //logic development using behavioral modelling
30 always@(*)
31 begin
32     if(SW[0] == 1)
33         out = 4'b0000;
34     else if(SW[1] == 1)
35         out = 4'b0001;
36     else if(SW[2] == 1)
37         out = 4'b0010;
38     else if(SW[3] == 1)
39         out = 4'b0011;
40     else if(SW[4] == 1)
41         out = 4'b0100;
42     else if(SW[5] == 1)
43         out = 4'b0101;
44     else if(SW[6] == 1)
45         out = 4'b0110;
46     else if(SW[7] == 1)
47         out = 4'b0111;
48     else if(SW[8] == 1)
49         out = 4'b1000;
50     else if(SW[9] == 1)
51         out = 4'b1001;
52     else
53         out = 4'bzzzz;
54 end
55
56 endmodule
57

```

- d. Investigate the design using Verilog test bench and simulations, and provide code screenshot.

```

58
59
60 module DEC_BCD_TB();
61 //Dimension and sizes
62 reg [9:0] SW;
63 wire [3:0] out;
64
65 //setting up data for simulation
66 initial
67 begin
68     #00 SW = 10'b0000000000;
69     #10 SW = 10'b0000000001;
70     #10 SW = 10'b0000000010;
71     #10 SW = 10'b0000000100;
72     #10 SW = 10'b0000001000;
73     #10 SW = 10'b0000010000;
74     #10 SW = 10'b0000100000;
75     #10 SW = 10'b0001000000;
76     #10 SW = 10'b0010000000;
77     #10 SW = 10'b0100000000;
78     #10 SW = 10'b1000000000;
79     #10 $finish;
80 end
81
82 //displaying data on TCL console
83 initial
84 begin
85     $display("Author: Malak Majeed Ullah khan\n");
86     $monitor($time,"ns input = %b, BCD output = %b",SW,out);
87 end
88
89 //instantiation
90 DEC_BCD DB0(out, SW);
91 endmodule
92

```

```


# run 1000ns
Author: Malak Majeed Ullah khan

      0ns input = 0000000000, BCD output = zzzz
     10ns input = 0000000001, BCD output = 0000
     20ns input = 0000000010, BCD output = 0001
     30ns input = 0000000100, BCD output = 0010
     40ns input = 0000001000, BCD output = 0011
     50ns input = 0000010000, BCD output = 0100
     60ns input = 0000100000, BCD output = 0101
     70ns input = 0001000000, BCD output = 0110
     80ns input = 0010000000, BCD output = 0111
     90ns input = 0100000000, BCD output = 1000
    100ns input = 1000000000, BCD output = 1001
$finish called at time : 110 ns : File "D:/FYP Slide/lab03/lab03.srcs/sources_1/new/DEC_BCD.v" Line 79
INFO: IUSE_VSim-961 VSim completed. Design snapshot 'DEC_BCD_TB_behav' loaded

```



 e. Investigate the design using Nexys 4 DDR hardware. Provide the constraint file screenshot and hardware output image.



2. Conflict arises in encoders when more than two inputs are activated simultaneously. This issue can be resolved by prioritising the either LSB or MSB inputs. This encoder is called priority encoder.

a. Design truth table for the decimal to BCD encoder.

Q NO 2

9	8	7	6	5	4	3	2	1	0	A ₃	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	x	0	0	0	1
0	0	0	0	0	0	0	1	x	x	0	0	1	0
0	0	0	0	0	0	1	x	x	x	0	0	1	1
0	0	0	0	0	1	x	x	x	x	0	1	0	0
0	0	0	0	1	x	x	x	x	x	0	1	0	1
0	0	0	1	x	x	x	x	x	x	0	1	1	0
0	0	1	x	x	x	x	x	x	x	0	1	1	1
0	1	x	x	x	x	x	x	x	x	1	0	0	0
1	x	x	x	x	x	x	x	x	x	1	0	0	1

b. Implement the design using Verilog behavioural modelling, and provide code screenshot.

```

22 // Malak Majeedullah khan
23
24 module DEC_priority_enc(Q, D);
25 //size and dimensions
26 input wire [9:0] D;
27 output reg [3:0] Q;
28
29 //logic for 8 bit priority encoder
30 always@ (D)
31 begin
32     casex(D)
33         10'b0000000001 : Q = 4'b0000;
34         10'b000000001x : Q = 4'b0001;
35         10'b00000001xx : Q = 4'b0010;
36         10'b0000001xxx : Q = 4'b0011;
37         10'b000001xxxx : Q = 4'b0100;
38         10'b00001xxxxx : Q = 4'b0101;
39         10'b0001xxxxxx : Q = 4'b0110;
40         10'b001xxxxxxx : Q = 4'b0111;
41         10'b01xxxxxxxx : Q = 4'b1000;
42         10'b1xxxxxxxxx : Q = 4'b1001;
43         default: Q = 4'bzzzz;
44     endcase
45 end
46 endmodule
47

```

c. Investigate the design using Verilog test bench and simulations, and provide code screenshot.

```

50 module DEC_priority_enc_TB();
51 //inputs and outputs for simulations
52 reg [9:0] D;
53 wire [3:0] Q;
54
55 //setting up values for simulation.
56 initial
57 begin
58     #00 D = 10'b0000000001;
59     #10 D = 10'b0000000010;
60     #10 D = 10'b0000000100;
61     #10 D = 10'b0000001000;
62     #10 D = 10'b0000010000;
63     #10 D = 10'b0000100000;
64     #10 D = 10'b0001000001;
65     #10 D = 10'b0010000001;
66     #10 D = 10'b0100000001;
67     #10 D = 10'b1000000001;
68     #10 $finish;
69 end
70
71 //displaying values on TCL-console
72 initial
73 begin
74     $display("Author: Malak Majeed ullah khan\n");
75     $monitor($time,"ns Input = %b, BCD_Output = %b", D, Q);
76 end
77
78 //instantiation
79 DEC_priority_enc DB0(Q, D);
80
81 endmodule

```


```

# run 1000ns
Author: Malak Majeed ullah khan

0ns Input = 0000000001, BCD_Output = 0000
10ns Input = 0000000010, BCD_Output = 0001
20ns Input = 0000000100, BCD_Output = 0010
30ns Input = 0000001000, BCD_Output = 0011
40ns Input = 0000010000, BCD_Output = 0100
50ns Input = 0000100000, BCD_Output = 0101
60ns Input = 0001000001, BCD_Output = 0110
70ns Input = 0010000001, BCD_Output = 0111
80ns Input = 0100000001, BCD_Output = 1000
90ns Input = 1000000001, BCD_Output = 1001

$finish called at time : 100 ns : File "D:/FYP Slide/lab03/lab03.srscs/sources_1/new/DEC_priority_enc.v" Line 68
INFO: [USF-XSim-96] XSim completed. Design snapshot 'DEC_priority_enc_TB_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 1000ns

```

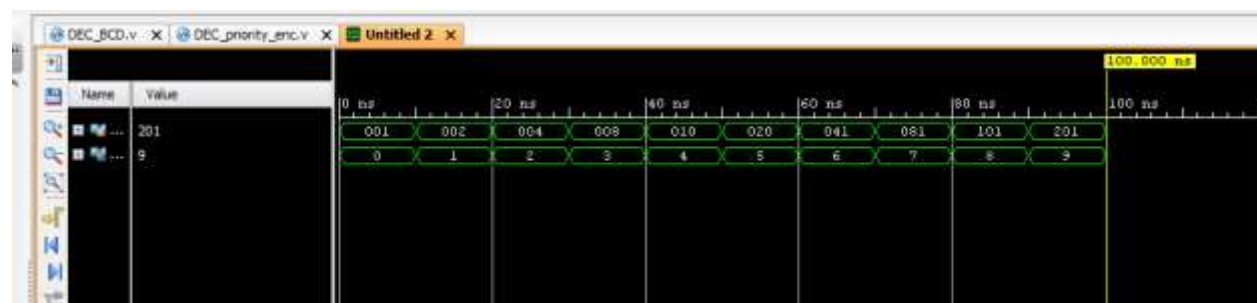

d. Investigate the design using Nexys 4 DDR hardware. Provide the constraint file screenshot and hardware output image.

